



Tolerances: Resistors $\pm 10\%$, Capacitors $\pm 20\%$, Voltages $\pm 5\%$

Fig. 79—Practical ring counter using