

FIGURE 35—Photography Light Meter.

The photodiode V1 must be polarized correctly. The cathode end of the photodiode is indicated by a red dot on body of the unit.

PARTS LIST

- | | |
|---|---|
| B1—9V. Battery, Burgess #2N6 with snap terminals or equivalent. | R2—27K, $\frac{1}{2}$ w. Resistor. |
| M1—Meter, 0 to 15 milliamperes D.C. | R3—250 Ω Potentiometer. |
| Q1—Sylvania 2N229 Transistor. | R4—68 Ω , $\frac{1}{2}$ w. Resistor. |
| R1—25K Potentiometer. | S1—S.P.S.T. Toggle Switch. |
| | V1—Sylvania 1N77A Photodiode. |

36. BINARY COUNTER

Description of Operation:

The binary counter consists of a cascade of flip-flop circuits containing indicator lights so that the state of each stage of the counter may be observed visually. The counter might be used by science or mathematics teachers for demonstrating binary addition or by students as part of a science fair display of computer type circuits. The circuit may be operated by a relay and be used to count objects moving on a conveyor belt or persons passing a photocell, etc.

The schematic diagram shows two stages but the counter may be extended to as many stages as desired. The counter counts from 0 to

$(2^N - 1)$, where N is the number of stages. The maximum count for a given number of counter stages is given in Table I.

N (number of counter stages)	$(2^N - 1)$
1	1
2	3
3	7
4	15
5	31
6	63
7	127
8	255
9	511
10	1023

TABLE I—Count capability as function of number of stages.

The counter operates as follows. Each time $S1$ is closed the flip-flop of stage 1 changes state. For example, if $Q1$ of stage 1 is conducting (lamp $I1$ lit), closing $S1$ causes a positive pulse to pass through $C1$ and

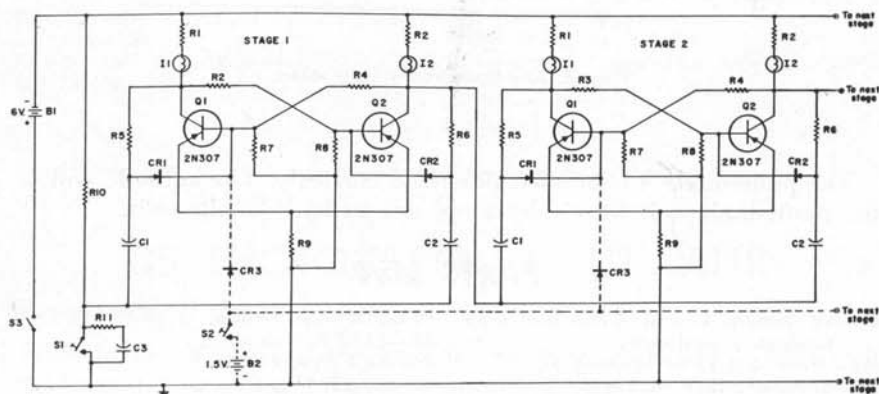


FIGURE 36—Binary Counter.

$CR1$ to the base of $Q1$ causing $Q1$ to be cut off and consequently $Q2$ to be turned on and lamp $I1$ to be lit. The positive pulse did not pass through $CR2$ because it was reverse biased through $R6$. The next time $S1$ is closed $Q2$ is turned off and $Q1$ turned on.

Each time $Q2$ of stage 1 is turned on the second counter stage changes state. Similarly each time $Q2$ of stage 2 is turned on stage 3 changes state. Thus the first stage changes state each time $S1$ is closed; the second stage changes state every second time $S1$ is closed; the third stage change state every fourth time $S1$ is closed, etc.

The way the count, or the number of times $S1$ has been closed, is displayed as shown in Table II.

Count	Stage 1		Stage 2		Stage 3	
	Lamp I1	Lamp I2	Lamp I1	Lamp I2	Lamp I1	Lamp I2
0	off	on	off	on	off	on
1	on	off	off	on	off	on
2	off	on	on	off	off	on
3	on	off	on	off	off	on
4	off	on	off	on	on	off
5	on	off	off	on	on	off
6	off	on	on	off	on	off
7	on	off	on	off	on	off
8	pattern	repeats				

TABLE II—Count display for 3 stage counter.

If one adapts the convention that lamp I2 of a particular stage being on represents 1 and Lamp I1 being off represents 0, then Table II may be written as shown in Table III. In Table III, the count is given in its binary representation written from right to left (least significant digit on right).

Count	Stage 1	Stage 2	Stage 3
0	0	0	0
1	1	0	0
2	0	1	0
3	1	1	0
4	0	0	1
5	1	0	1
6	0	1	1
7	1	1	1
8	pattern	repeats	

TABLE III—Binary representation of count (least significant digit on right).

Table III (and also correspondingly Table II) may be extended to an additional stage 4 by repeating the pattern for the two stages shown to give 15 count positions and in the stage 4 column writing 0's to count 7 and 1's to count 15. In this manner the table may be extended to any number of stages.

In the schematic diagram the part of the circuit shown in dotted lines (containing S2, B2 and diode CR3) may be included to reset the counter to zero by closing S2 momentarily.

The power dissipation in the transistors is low and they need not be mounted on a heat sink.

PARTS LIST

- B1—6V. Battery, Burgess F4BP or equivalent.
 B2—1.5V. Battery, Burgess #2R or equivalent.
 C1, C2—.047 or .05 Mfd. Paper or Ceramic Capacitor.
 C3—.1 Mfd. Paper Capacitor.
 CR1, CR2, CR3—1N34A Diode.
 I1, I2—Sylvania #48 or #49 2V., 60 ma. Pilot Lamp.
 Q1, Q2—Sylvania 2N307 Transistors.
 R1, R2—68 Ω , 1/2 w. Resistor.
 R3, R4, R7, R8—1.2K 1/2 w. Resistor.
 R5, R6, R10—10K, 1/2 w. Resistor.
 R9—4.7 Ω 1/2 w. Resistor.
 R11—27 Ω 1/2 w. Resistor.
 S1—Switch, normally open momentary contact pushbutton type such as Grayhill Type 2201 or equivalent.
 S2—Same as S1.
 S3—S.P.S.T. Toggle Switch.
 NOTE: C1, C2, R1 through R9, CR1, CR2, CR3, I1, I2, Q1, Q2 must be duplicate for each stage used.